

CS 250 Lab 1 Grading Form

Name: _____

1. Truth table (20 pts)

A	B	C	Out
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	
1	0	1	
1	1	0	
1	1	1	

2. Boolean Expression for 3-input NAND gate (20pts)

3. Circuit works properly (40pts)

4. Board looks nice and wires are straight (20pts)

Grader : _____